

Multivibrators

* Non-linear circuits used to produce various signals like square or triangular waves.

1

Types of multivibrators

Bistable	Monostable	Astable
\Rightarrow Could be at one of two stable states indefinitely and only moves to the other state when it's appropriately triggered.	\Rightarrow Has one stable state. \Rightarrow Resides at the stable state in ordinary conditions, moves to the instable state when triggered for a specific interval then comes back to S.S.	\Rightarrow Doesn't have any stable state. \Rightarrow Stays at one of two levels for a period of time, then moves to the other level for another period and the process is repeated. (Quasi-Stable states)

1 Bistable Multivibrators

* The feedback loop:

\Rightarrow Large open-loop gain (A).

$$\Rightarrow V_+ = V_o \frac{R_1}{R_1 + R_2} = \beta V_o$$


\Rightarrow Consider noise signal at V_+ terminal with small +ve value;

Noise amplified by the large gain (A).

$\therefore V_o$ increases with (+ve) value

$\therefore V_+ = \beta V_o \Rightarrow \therefore V_+ \rightarrow +ve$ value

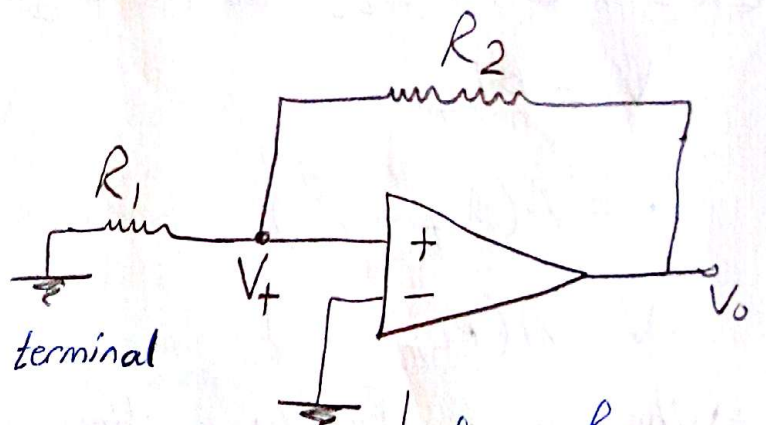When $AB > 1 \Rightarrow V_+$ is amplified again



$$\beta = \frac{R_1}{R_1 + R_2}$$

$$V_o = A(V_+ - V_-)$$

V_o increases until it reaches the saturation level

$$\therefore V_o = L_+ \text{ (+ve saturation level)}$$

→ 1st stable state

⇒ If noise signal is (-ve) value at the beginning:

$$V_o = A(V_+ - V_-) \rightarrow V_o \text{ is (-ve) \& decreases}$$

$\swarrow \text{-ve} \quad \searrow \rightarrow 0$

V_o continues to decrease till it reaches -ve saturation level.

$$V_o = L_-$$

→ 2nd stable state.

⇒ Note that the circuit can't exist in the state for which $(V_+ = 0 \text{ \& } V_o = 0)$ for any period of time.

*Transfer Characteristics of inverting Bistable Multivibrator:

① Consider $V_o = L_+$ at the beginning:


$$V_+ = \beta L_+$$

$$V_o = A(V_+ - V_-)$$

$$\therefore V_o = A(\beta L_+ - V_i)$$

⇒ When V_i is firstly applied & has a small value, it'll have no effect on the output.

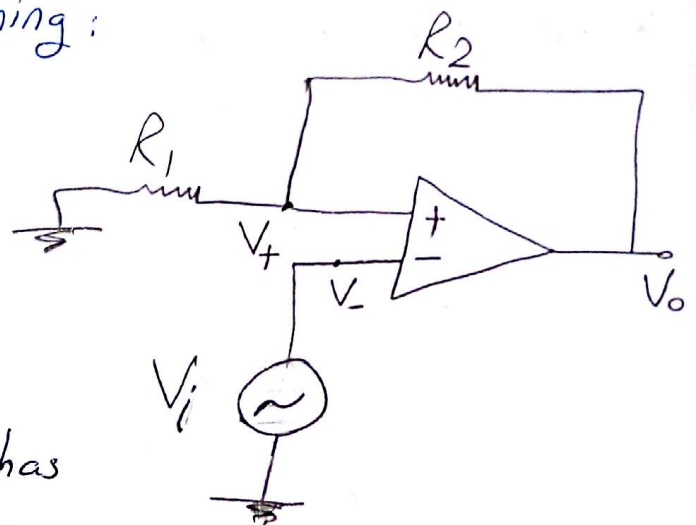⇒ When $V_i = \beta L_+$ & begins to exceed this value: $V_o = A(\beta L_+ - V_i)$
 $\therefore V_o$ becomes negative




$V_o = L_-$ (other stable state)

⇒ At this point of transition:

$$V_i = V_{TH}$$

↳ High Threshold Voltage

$$V_+ = \beta L_-$$

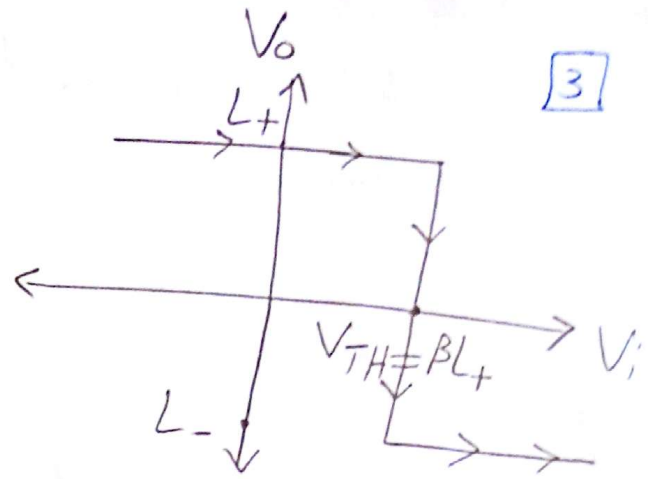

② The case now is: $V_o = L_-$ & V_i will start to decrease
 $V_+ = \beta L_-$ (-ve value)

⇒ If V_i increases, no effect on the output.

⇒ If V_i decreases until $V_i = \beta L_-$ & decreases more

$$V_o = A(\beta L_- - V_i)$$

↳ +ve


∴ V_o goes +ve again

$$V_o = L_+$$


$$V_+ = \beta L_+$$

⇒ At this point of transition:

$$V_i = V_{TL} = \beta L_-$$

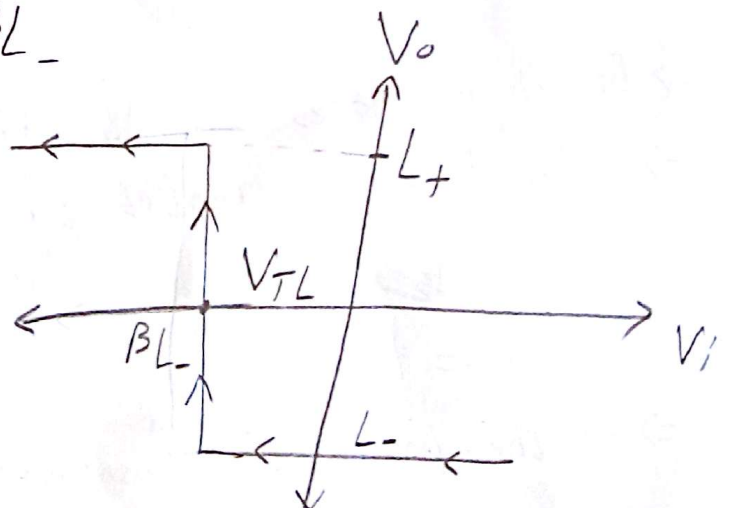


The total Ch/c can be drawn as follows:

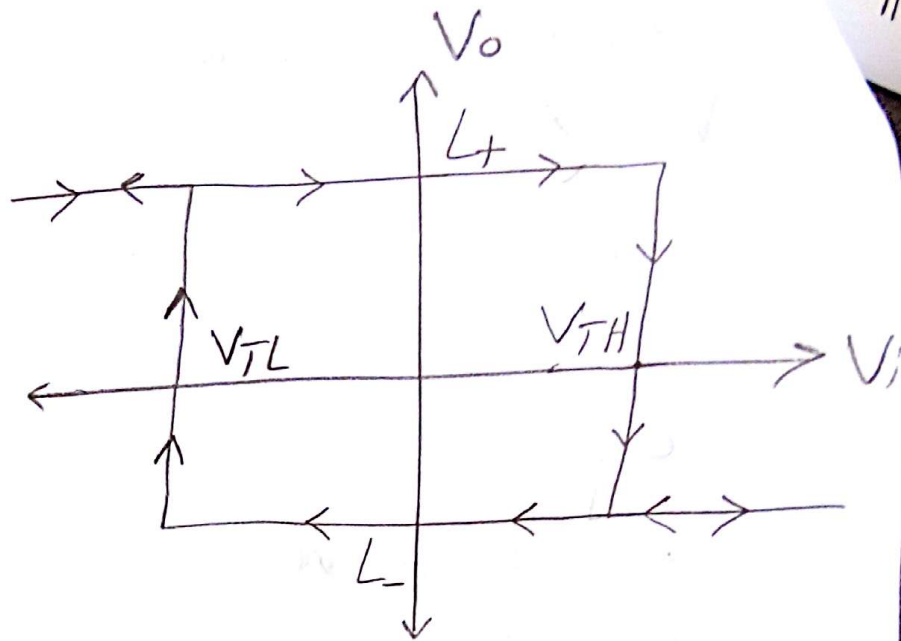

* Transfer Ch/c for non-inverting Bistable:

⇒ The voltage V_+ can be obtained using superposition:
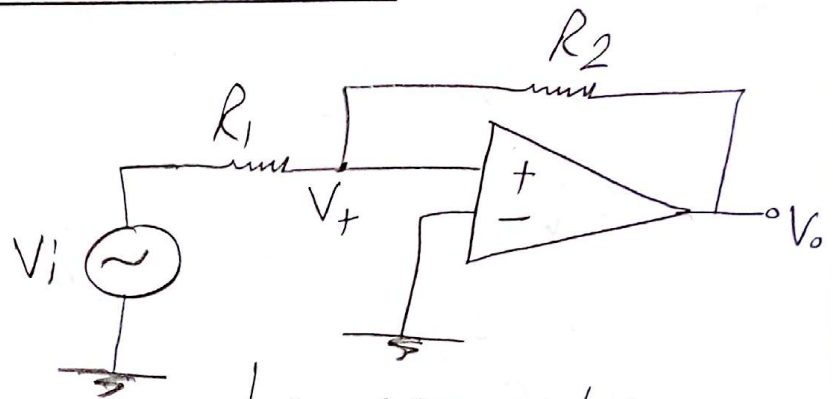
$$V_+ = V_o \frac{R_1}{R_1 + R_2} + V_i \frac{R_2}{R_1 + R_2}$$



① Consider $V_o = L_+$ at the beginning:

$$V_+ = L_+ \frac{R_1}{R_1 + R_2} + V_i \frac{R_2}{R_1 + R_2}$$

$$\begin{aligned} V_o &= A(V_+ - V_-) \\ &\rightarrow 0 \\ \therefore V_o &= AV_+ \end{aligned}$$

⇒ If V_i increases ⇒ No effect

⇒ If V_i decreases until the total $V_+ = \text{Zero}$

∴ V_o switches to the other state

$$V_o = L_-$$

⇒ At the point of transition: $V_+ = 0$

$$\therefore V_i \frac{R_2}{R_1 + R_2} = -L_+ \frac{R_1}{R_1 + R_2} \Rightarrow V_i = V_{TL} = -L_+ \frac{R_1}{R_2}$$

② Now $V_o = L_-$ & $V_+ = L_- \frac{R_1}{R_1 + R_2} + V_i \frac{R_2}{R_1 + R_2}$; 5


⇒ IF V_i decreases → No effect.

⇒ IF V_i increases until $V_+ = \text{Zero}$, V_o switches to the +ve saturation level.
 $\therefore V_o = L_+$


⇒ At this point of transition: $V_i \frac{R_2}{R_1 + R_2} = -L_- \frac{R_1}{R_1 + R_2}$

$$\therefore V_i = V_{TH} = -L_- \frac{R_1}{R_2}$$

* The Ch/c can be drawn:

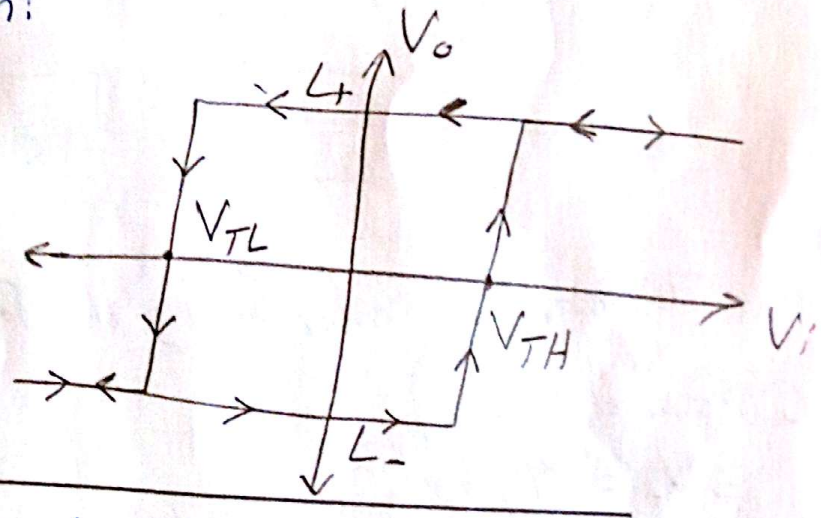


* Making the output level more precise:

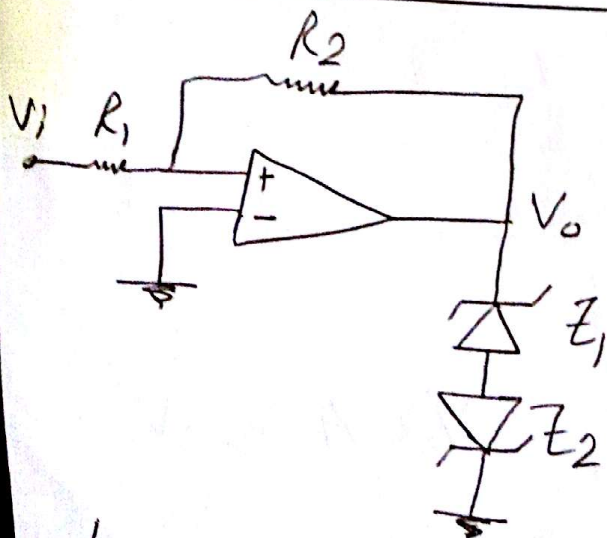

$$L_+ = V_{Z_1} + V_{D_2}$$

$$L_- = -(V_{D_1} + V_{Z_2})$$

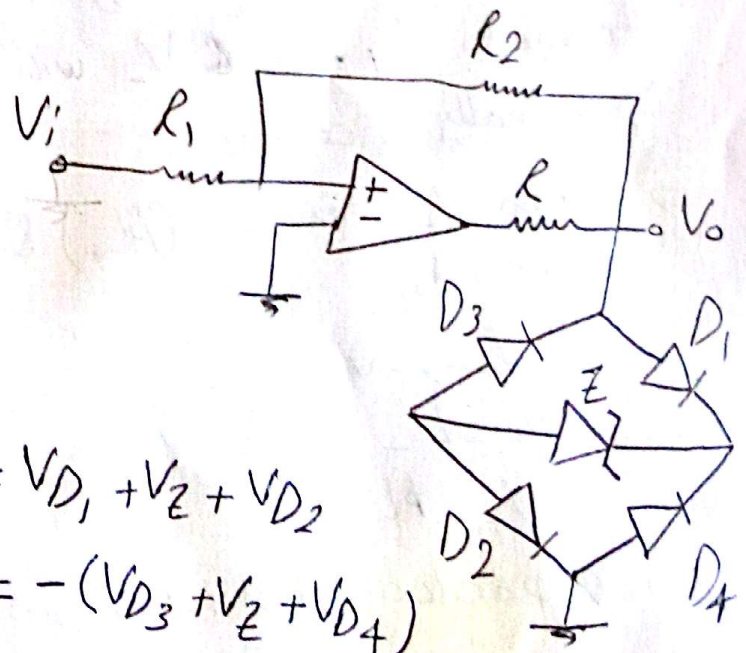


$$L_+ = V_{D_1} + V_Z + V_{D_2}$$

$$L_- = -(V_{D_3} + V_Z + V_{D_4})$$

2] Astable Multivibrators:-

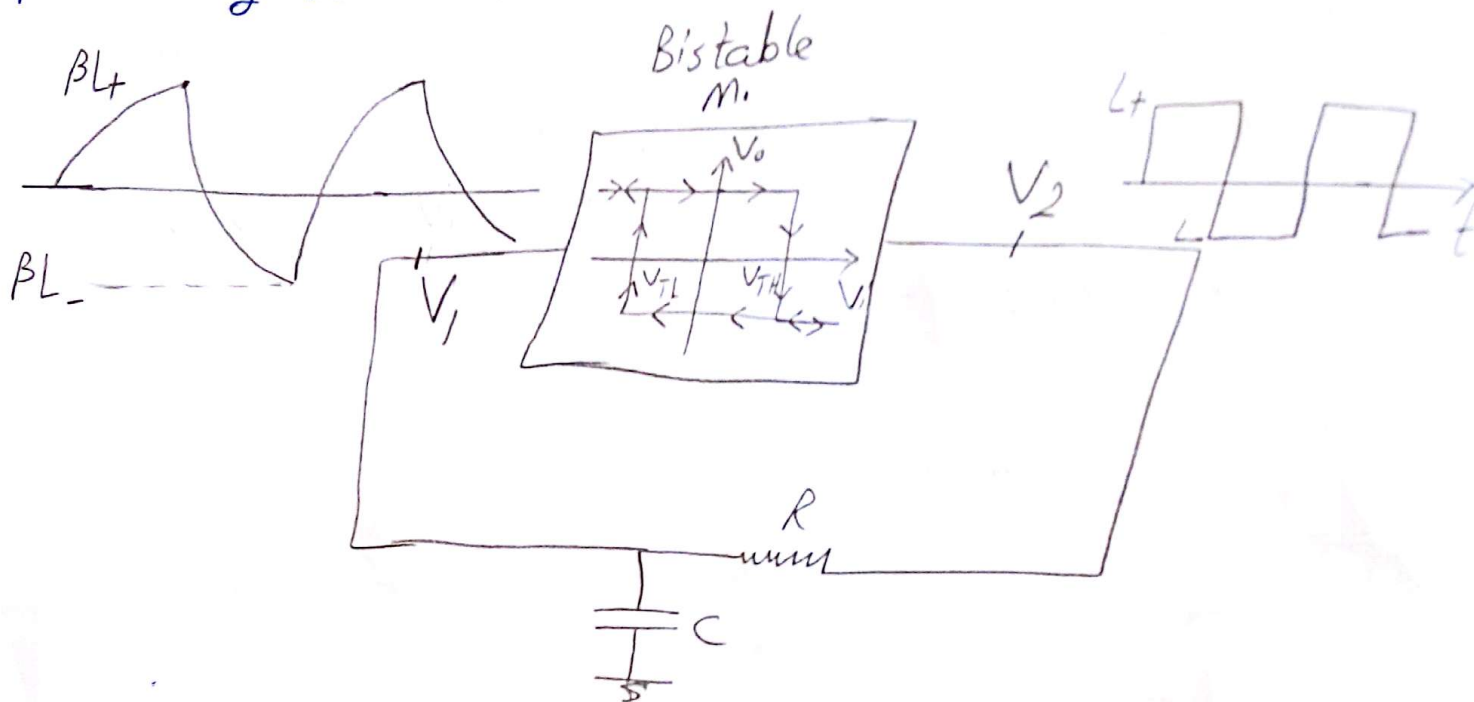* The bistable multivibrator can be arranged to switch periodically between the two states & become an astable M.



* This can be realized by the following circuit:

① Assume $V_0 = L_+$:

$$\Rightarrow V_+ = \beta L_+$$

\Rightarrow Capacitor C will charge towards L_+ , so V_- will gradually increase.


\Rightarrow When V_- reaches (βL_+) & exceeds,

$$: V_0 \rightarrow -ve$$

$$V_0 = L_-$$

$$: V_+ = \beta L_-$$

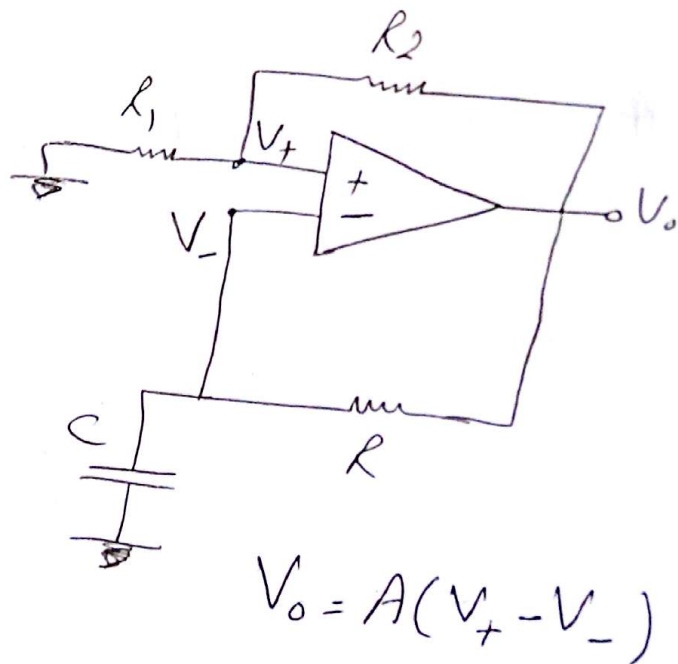\Rightarrow Capacitor will discharge through R



$\therefore V_-$ gradually decreases until $V_- = \beta L_-$

7

\Rightarrow When V_- decreases beyond (βL_-)

$\therefore V_o \rightarrow +ve$

$$V_o = L_+$$

Capacitor charges again.

* The time constant for charging & discharging:

$$\tau = RC$$

\Rightarrow The process is repeated periodically with a period $= T$

$$T = T_1 + T_2$$


$$\Rightarrow T_1 = \tau \ln \left(\frac{1 - \beta \left[\frac{L_-}{L_+} \right]}{1 - \beta} \right)$$

$$\Rightarrow T_2 = \tau \ln \left(\frac{1 - \beta \left[\frac{L_+}{L_-} \right]}{1 - \beta} \right)$$

$$\therefore L_+ = -L_-$$

$$\therefore T = T_1 + T_2$$
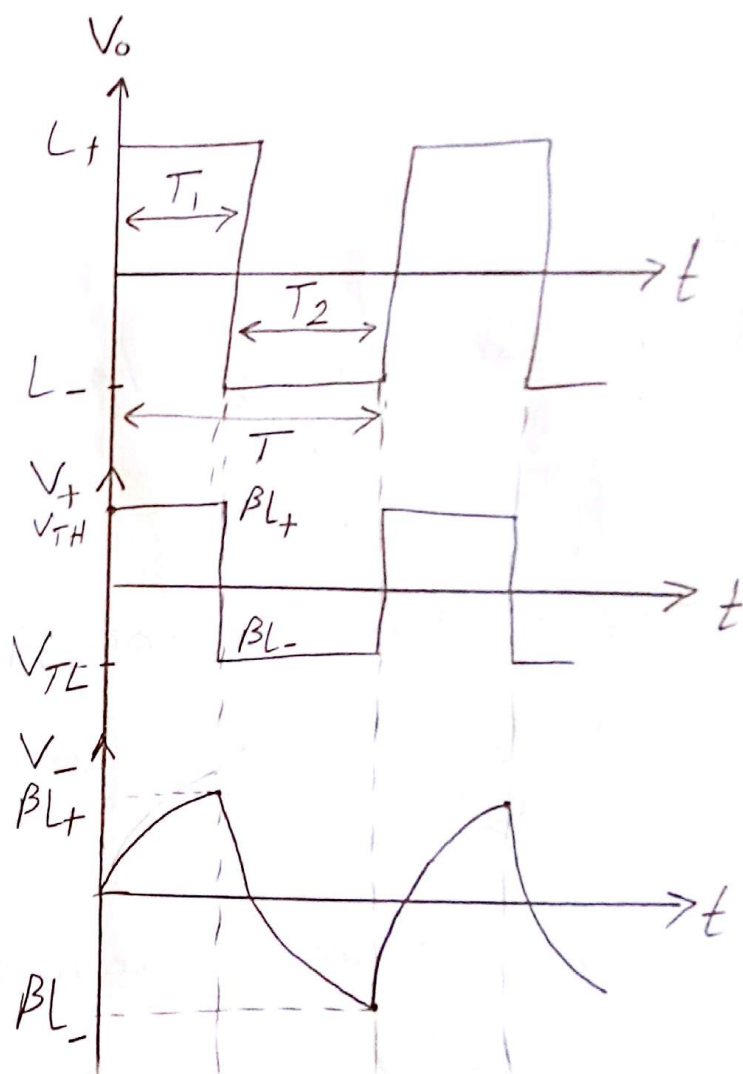
$$\therefore T = 2\tau \ln \left(\frac{1 + \beta}{1 - \beta} \right)$$



* **Note**: The general equation for the capacitor voltage when charging & discharging through R is:


$$v(t) = V_{\infty} - (V_{\infty} - V_{0+}) e^{-t/\tau} \rightarrow RC$$

Final voltage \swarrow

\searrow Voltage at $t=0+$ (the beginning)

* Generation of triangular waveform:-

8

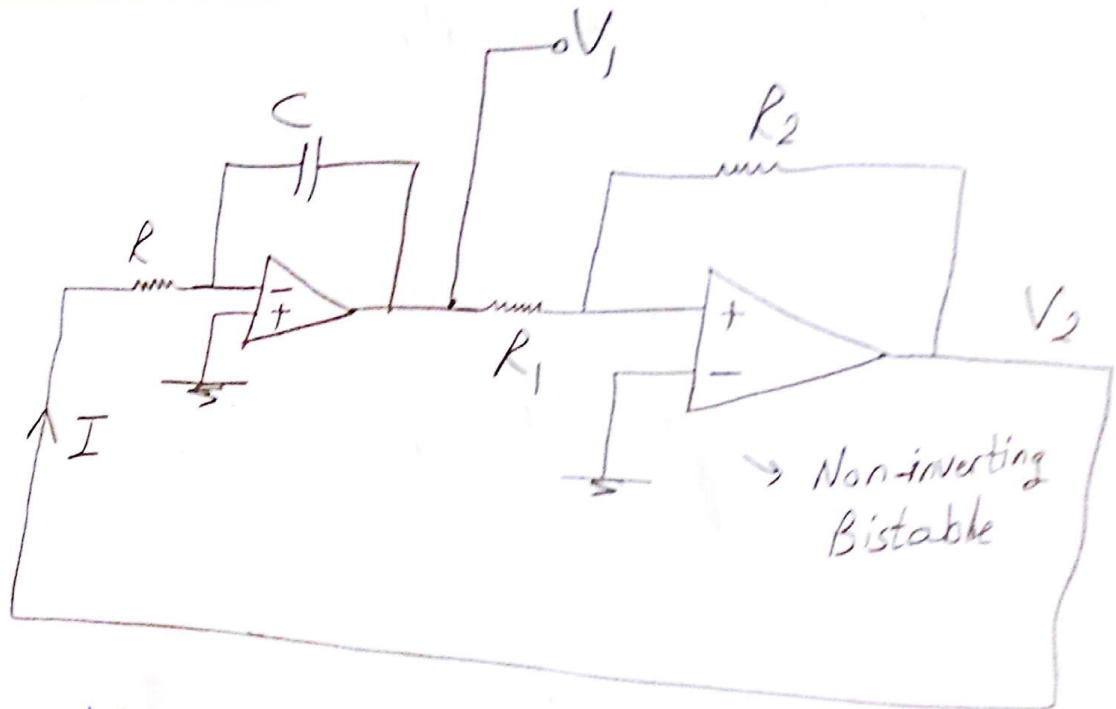

① Assume $V_2 = L_+$

⇒ The current passing through the capacitor will be:

$$I = \frac{L_+}{R}$$

⇒ O/P of the integrator decreases with a slope = $-\frac{L_+}{RC}$

⇒ O/P of integrator is the i/P for the multivibrator.

↳ V_1

⇒ V_1 continues to decrease until $V_1 = V_{TL}$

$$\therefore V_2 = L_-$$

② $V_2 = L_- \rightarrow (-ve \text{ value})$

∴ V_1 increases with a slope = $-\frac{L_-}{RC}$

V_1 continues to increase until $V_1 = V_{TH}$

$$\therefore V_2 = L_+$$

8

$$\Rightarrow T_1 = RC \frac{V_{TH} - V_{TL}}{L_+}$$

$$\Rightarrow T_2 = RC \frac{V_{TH} - V_{TL}}{L_-}$$

$$\Rightarrow V_{TH} = -L_- \frac{R_1}{R_2}, V_{TL} = -L_+ \frac{R_1}{R_2}$$

$$L_+ = -L_-$$

$$\Rightarrow \therefore T = T_1 + T_2$$

$$T = 4RC \frac{R_1}{R_2}$$

$$\therefore f = \frac{1}{4RC} \frac{R_1}{R_2}$$

9

